

APPLICATION NOTE

Using Coaxial Line Elements as Inductors

Introduction

Coaxial line elements can be used below resonance to simulate high Quality factor (Q), temperature-stable, compact inductors. More precisely, shorted coaxial lines exhibit an inductive reactance when used below quarter-wave resonance, and approximate the behavior of an ideal inductance or coil over a limited frequency range. As the operating frequency approaches the Self-Resonant Frequency (SRF) of the coaxial line element, the approximation is less valid.

An exact equivalent circuit is complex and includes parasitic elements resulting from a transition from the printed wiring board to the interior of the coaxial line. In this Application Note, a first-order model includes only the ceramic coaxial line and an estimate of the inductance due to the physical length of the center conductor tab. The tab inductance appears in series with the coaxial line's input impedance. An ideal, loss-less transmission line is assumed to simplify the calculations. Minor corrections to part length may be evident from prototype circuit performance.

Let the preferred inductive reactance at the design frequency (f_0) be approximated by:

$$Z_{input} = Z_0 \tan(\Theta) \quad (1)$$

Where:

- Z_{input} = Impedance at the coaxial line terminals (Ω).
- Z_0 = Coaxial line characteristic impedance (Ω).
- Θ = $\frac{2\ell}{\lambda_g}$ Coaxial electrical length (radians).

The characteristic impedance (Z_0) is established by the coaxial dimensions and the material dielectric constant (ϵ_r), as shown in Table 1. The cross-section width (W) and hole diameter (d) differ from final catalog part sizes by an allowance of 0.001 inches for conductor metallization thickness.

Table 1. Coaxial Lines Properties vs Profile and Material

Profile	1000 (10.5 ± 0.5)	2000 (20.6 ± 1.0)	8800 (39.0 ± 1.5)	9000 (90 ± 3)	Tab Inductors
HP	25.3 Ω	18.1 Ω	13.1 Ω	8.6 Ω	1.8 nH
EP	22.5 Ω	16.1 Ω	11.7 Ω	7.7 Ω	1.0 nH
SP	18.3 Ω	13.1 Ω	9.5 Ω	6.3 Ω	1.0 nH
LS	18.4 Ω	13.1 Ω	9.5 Ω	6.3 Ω	0.9 nH
LP	27.4 Ω	19.6 Ω	14.2 Ω	9.4 Ω	1.0 nH
SP	25.7 Ω	18.4 Ω	13.3 Ω	8.8 Ω	0.6 nH
SM	18.4 Ω	13.1 Ω	9.5 Ω	6.3 Ω	0.6 nH

The Z_0 values in Table 1 were computed from the following approximation from H. Riblet's *An Accurate Approximation of the Impedance of a Circular Cylinder Concentric with an External Square Tube*, IEEE Transactions on Microwave Theory and Techniques, Volume MTT-31, October 1983, pp. 841–844.

$$Z_0 = \frac{60}{\sqrt{\epsilon_r}} \ln\left(1.079 \frac{W}{d}\right) \quad (2)$$

- Z_0 = Coaxial line characteristic impedance (Ω).
- ℓ = Coaxial line physical length (inches).
- ϵ_r = Material dielectric constant.
- W = Cross-section width (inches).
- d = Hole diameter (inches).

The wavelength in the dielectric (λ_g) can be calculated from the expression in Table 2, with f_0 as the design frequency in MHz.

Table 2. Wavelength (λ_g) in Dielectric

Material	ϵ_r	Wavelength Formula for λ_g (Inches)
1000	10.5 ± 0.5	3642/ f_0
2000	20.6 ± 1.0	2601/ f_0
8800	39.0 ± 1.5	1890/ f_0
9000	90 ± 3	1244/ f_0

$$\iota = \frac{\lambda_g}{2\pi} \tan^{-1}\left(\frac{Z_{input}}{Z_0}\right) \quad (3)$$

- ι = Length of part (inches).
- λ_g = Wavelength in the dielectric at f_0 (inches).
- Z_{input} = Impedance at the coaxial line terminals (Ω).
- Z_0 = Coaxial line characteristic impedance (Ω).

Note: The shorted transmission line model requires the constant of the material filling the coaxial line.

Inductance-per-unit/length formulas are useful only when the line is very short compared to a wavelength, and are inaccurate as the f_0 approaches the SRF. The equation for input impedance can be rearranged to determine the part length for a preferred inductive reactance.

APPLICATION NOTE • USING COAXIAL LINE ELEMENTS AS INDUCTORS

The SRF must lie within the recommended frequency range for the same profile and material when used as a coaxial resonator. This restriction places constraints upon the range of inductive reactance that can be realized by this technique, although arbitrarily high reactance values can be achieved close to the SRF. The designer should carefully analyze the circuit response when the f_0 is near the SRF.

The SRF can be calculated from previously-determined values. The center conductor tab presents a small additional series inductance that may be included in the total preferred inductive reactance. Although the tab influence has not been measured, the suggested approximate values are given in Table 1.

The SRF can be calculated from:

$$\text{SRF} = \frac{\lambda_g f_0}{4} \times \frac{1}{l} \quad (4)$$

Where:

- λ_g = Wavelength in the dielectric at f_0 (inches).
- f_0 = Design frequency (MHz).
- l = Coaxial physical length (inches).

Copyright © 2013, Trans-Tech Inc., Inc. All Rights Reserved.

Information in this document is provided in connection with Trans-Tech, Inc. ("Trans-Tech"), a wholly-owned subsidiary of Skyworks Solutions, Inc. These materials, including the information contained herein, are provided by Trans-Tech as a service to its customers and may be used for informational purposes only by the customer. Trans-Tech assumes no responsibility for errors or omissions in these materials or the information contained herein. Trans-Tech may change its documentation, products, services, specifications or product descriptions at any time, without notice. Trans-Tech makes no commitment to update the materials or information and shall have no responsibility whatsoever for conflicts, incompatibilities, or other difficulties arising from any future changes.

No license, whether express, implied, by estoppel or otherwise, is granted to any intellectual property rights by this document. Trans-Tech assumes no liability for any materials, products or information provided hereunder, including the sale, distribution, reproduction or use of Trans-Tech products, information or materials, except as may be provided in Trans-Tech Terms and Conditions of Sale.

THE MATERIALS, PRODUCTS, AND INFORMATION ARE PROVIDED "AS IS" WITHOUT WARRANTY OF ANY KIND, WHETHER EXPRESS, IMPLIED, STATUTORY, OR OTHERWISE, INCLUDING FITNESS FOR A PARTICULAR PURPOSE OR USE, MERCHANTABILITY, PERFORMANCE, QUALITY, OR NON-INFRINGEMENT OF ANY INTELLECTUAL PROPERTY RIGHT; ALL SUCH WARRANTIES ARE HEREBY EXPRESSLY DISCLAIMED. TRANS-TECH DOES NOT WARRANT THE ACCURACY OR COMPLETENESS OF THE INFORMATION, TEXT, GRAPHICS, OR OTHER ITEMS CONTAINED WITHIN THESE MATERIALS. TRANS-TECH SHALL NOT BE LIABLE FOR ANY DAMAGES, INCLUDING BUT NOT LIMITED TO ANY SPECIAL, INDIRECT, INCIDENTAL, STATUTORY, OR CONSEQUENTIAL DAMAGES, INCLUDING WITHOUT LIMITATION, LOST REVENUES OR LOST PROFITS THAT MAY RESULT FROM THE USE OF THE MATERIALS OR INFORMATION, WHETHER OR NOT THE RECIPIENT OF MATERIALS HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGE.

Trans-Tech products are not intended for use in medical, lifesaving, or life-sustaining applications, or other equipment in which the failure of the Trans-Tech products could lead to personal injury, death, or physical or environmental damage. Trans-Tech customers using or selling Trans-Tech products for use in such applications do so at their own risk and agree to fully indemnify Trans-Tech for any damages resulting from such improper use or sale.

Customers are responsible for their products and applications using Trans-Tech products, which may deviate from published specifications as a result of design defects, errors, or operation of products outside of published parameters or design specifications. Customers should include design and operating safeguards to minimize these and other risks. Trans-Tech assumes no liability for applications assistance, customer product design, or damage to any equipment resulting from the use of Trans-Tech products outside of stated published specifications or parameters.